

نظم القياس الإلكترونية

Electronic Measurement Systems

(EMS)

كلية الهندسة الكهربائية والالكترونية - جامعة حلب
د. أسعد كعدان

المحاضرة 7 - القياسات التفاضلية والمترابطة


مصادر المحاضرة

- Electronic Instrumentation, Prof. Dr. Kofi Makinwa
<https://ocw.tudelft.nl/courses/electronic-instrumentation/>
 - Lecture 4 - Differential Measurements and Responses of Amplifiers to common-mode signals
- Electronic Instrumentation, Prof. Dr. Kofi Makinwa
<https://ocw.tudelft.nl/courses/electronic-instrumentation/>
 - Lecture 6 - Coherent detection

- **Differential (as opposed to single-ended) measurements have many advantages:**
 - inherently reject common-mode interference and noise
 - allow a wider swing for a fixed power-supply voltage
 - minimize offset and even order distortion
 - (in some cases) lead to improved sensor linearity
- **BUT most practical amplifiers also respond to some degree to common-mode signals**
 - The appropriate figure of merit is the common-mode rejection ratio (**CMRR**).
 - Good amplifiers can achieve CMRRs > 120dB


Differential Amplifiers

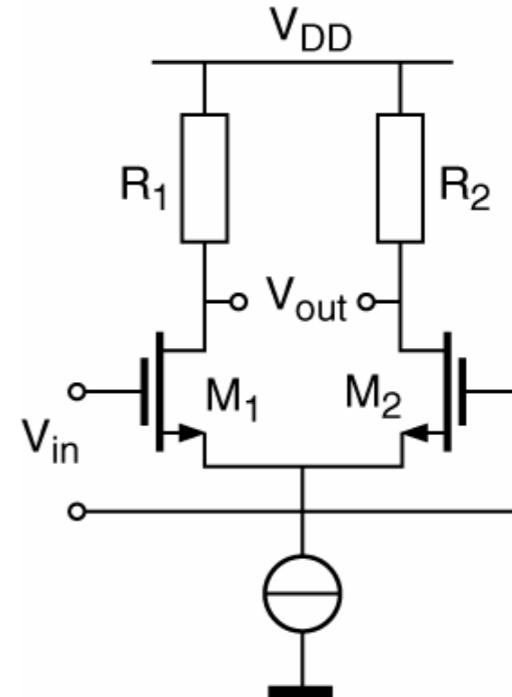- Widely used to amplify DC signals
- Balanced structure is
- Nominally offset free
- Rejects common-mode and power supply interference
- Easily realized in both CMOS and bipolar technologies




Practical Diff. Amps

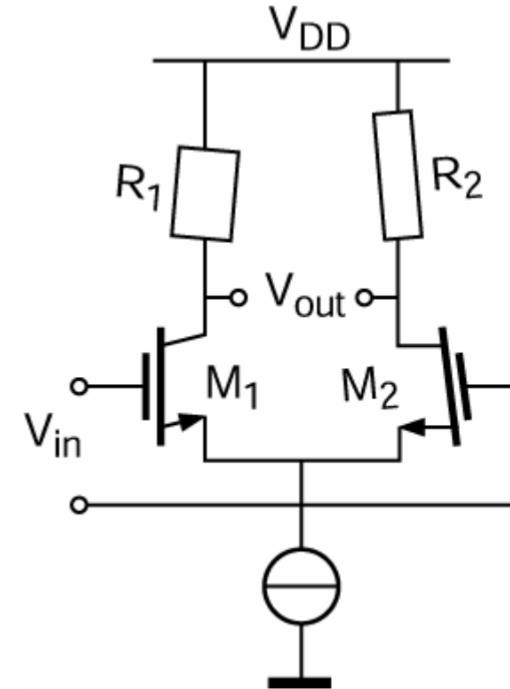- Component mismatch e.g.
 $R_1 \neq R_2$, $M_1 \neq M_2$
 \Rightarrow offset, finite CMRR & PSRR
- Mismatch is mainly due to
 - Process variation
 - Lithographic errors
- All things being equal:
 - CMOS amplifiers are 10x worse than Bipolar amplifiers



A differential measurement is characterized by a (small) differential signal of interest, which is superimposed on a (large) common-mode signal.

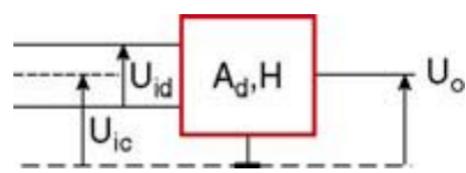The differential measurement should be sensitive to the differential signal only, regardless of the magnitude of the common-mode signal. The extent to which this is achieved by the read-out is by the common-mode rejection (**CMRR or H**).



$$H = \frac{A_d}{A_c} = \frac{\frac{U_o}{U_{id}}}{\frac{U_o}{U_{ic}}} = \left(\frac{U_{ic}}{U_{id}} \right)_{Uo=const}$$

Ideally: $U_o = A_d U_{id}$, but practically: $U_o = A_d(U_{id} + U_{ic}/H)$.

The term U_{ic}/H is an error signal, so H should be maximized.

Note: Reader uses “ G_d ” rather than “ A_d “

ECG



= small differential biopotential
 $U_{id} \sim 10 \mu\text{V}$ (0 - 100 Hz)

Superimposed on a large
 common-mode mains voltage
 $U_{ic} \sim 1 \text{ mV}$, 50 Hz.

Application requires:


1. High CMRR > 80dB
 (Filtering not possible)
2. High input impedance
 (electrode impedances R_s
 are not well defined)

⇒ Instrumentation Amplifier

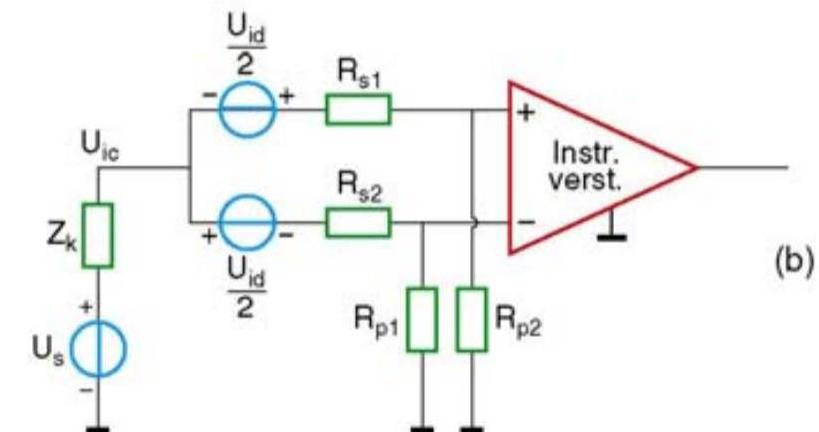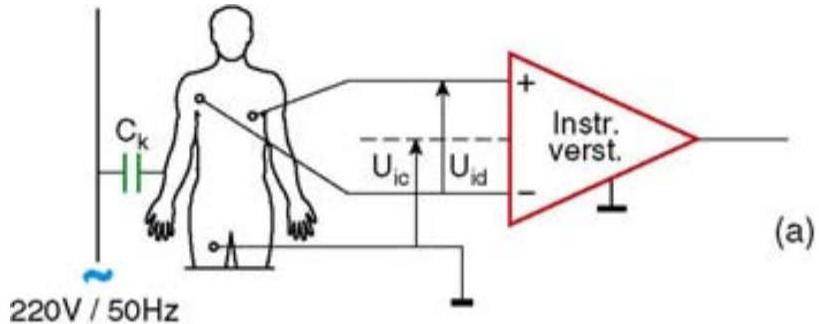

Achieving higher CMRR (1)


ET8.017
El. Instr.

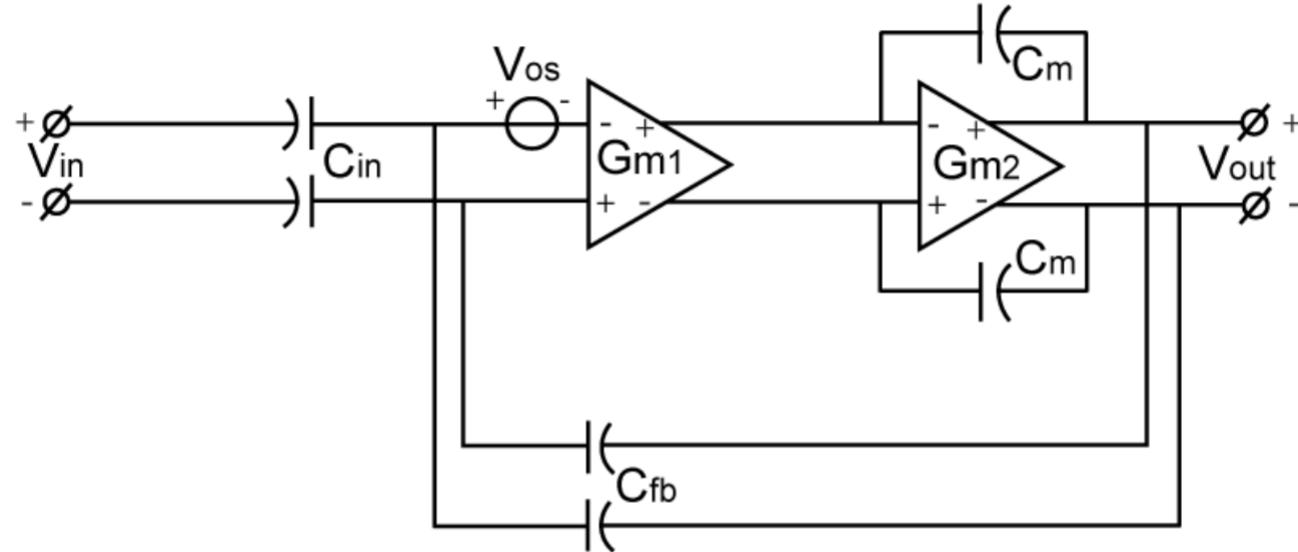

- Capacitors will block the common-mode voltage
 \Rightarrow a capacitively coupled amplifier? Closed-loop gain?
- Two stage amplifier \Rightarrow high open-loop DC gain (> 100dB)
- DC stability?


Achieving higher CMRR (2)

ET8.017
El. Instr.

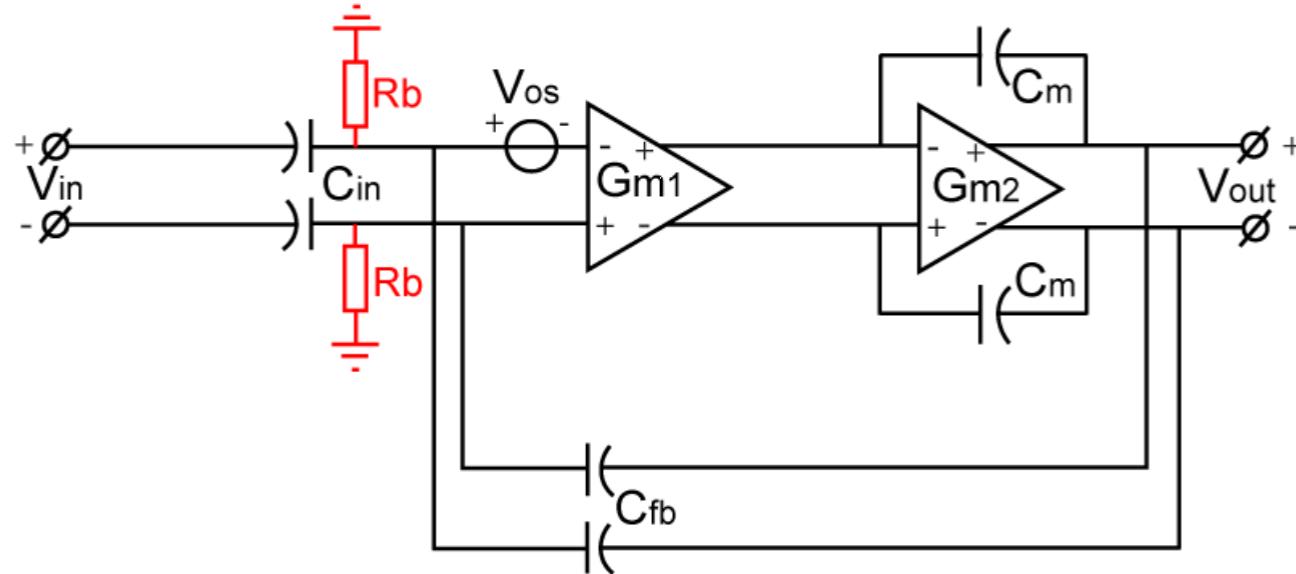

- Extra resistors are needed to establish DC voltages
- Trade-off: should be quite large ($M\Omega$) to minimize noise, should be small to minimize CM settling time
- DC closed-loop gain?


Achieving higher CMRR (3)

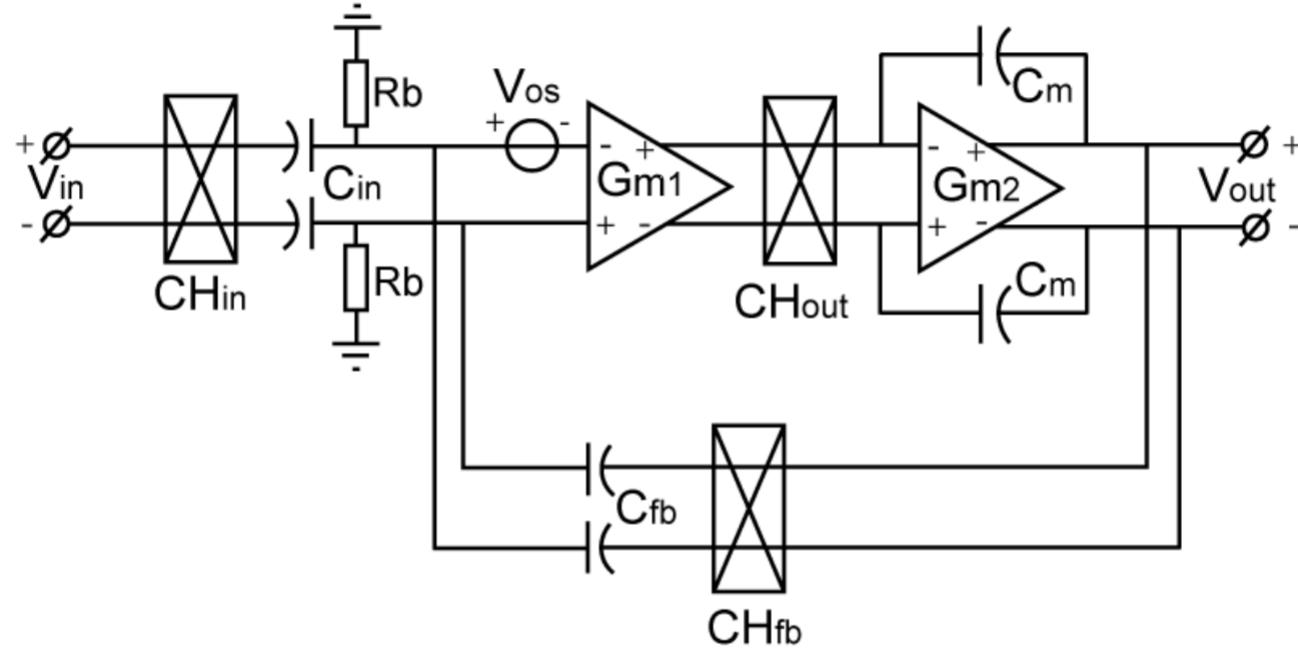

- Polarity reversing switches (known as choppers) convert input DC signals into AC signals (square-waves)
- To maintain feedback polarity, the feedback path and the amplifier also contain choppers

Achieving higher CMRR (4)

ET8.017
El. Instr.

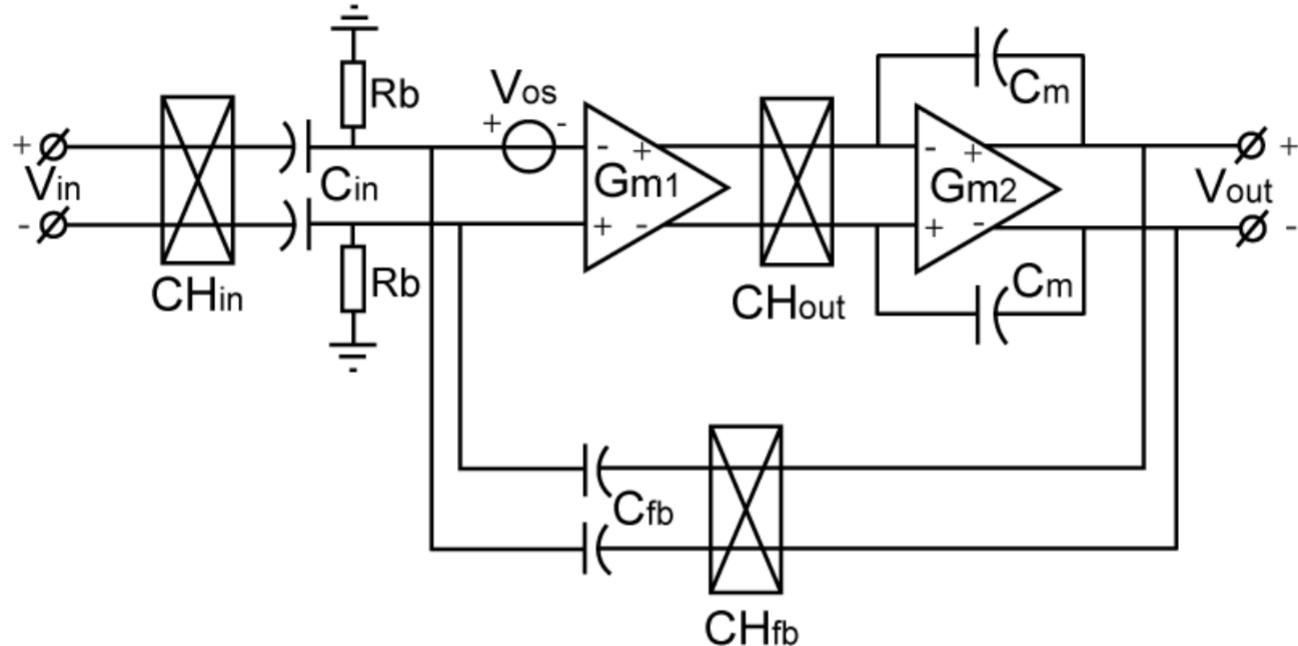

- Result: 1 μ V offset, 0.16% gain error, 134dB CMRR, 120dB PSRR

Q. Fan, F. Sebastian, J.H. Huijsing and K.A.A. Makinwa, "A 1.8 μ W 1 μ V-Offset Capacitively-Coupled Chopper Instrumentation Amplifier in 65nm CMOS," *J. Solid-State Circuits*, vol. 46, is. 7, pp. 1534 - 1543, July 2011.

- A close cousin of CMRR is the power-supply rejection ratio (PSRR), which expresses how sensitive the amplifier is to changes in its supply voltage.

$$PSRR = \frac{A_d}{A_{sy}} = \frac{\frac{U_o}{U_{id}}}{\frac{U_o}{\Delta U_{sy}}} = \left(\frac{\Delta U_{sy}}{U_{id}} \right)_{Uo=const}$$

- Here ΔU_{sy} represents the changes in the supply voltage
- A good instrumentation amplifier will have a $PSRR > 100dB$

- Synonyms: coherent detection, synchronous demodulation, lock-in amplification, chopping??
- These are all modulation techniques that are used to improve the low frequency performance of measurement systems
- When square-wave modulation is employed, the technique is referred to as chopping


When to use it?

- When measuring low-bandwidth or quasi-static signals in the presence of high noise or disturbance levels.
- If a high dynamic range is required

Therefore it is often used to readout sensors e.g.

- (MEMS) Accelerometers (fF capacitance changes)
- Optical (infrared) detectors (fA's of current)
- Magnetic sensors (mV's)
- Strain gauges (mV's)

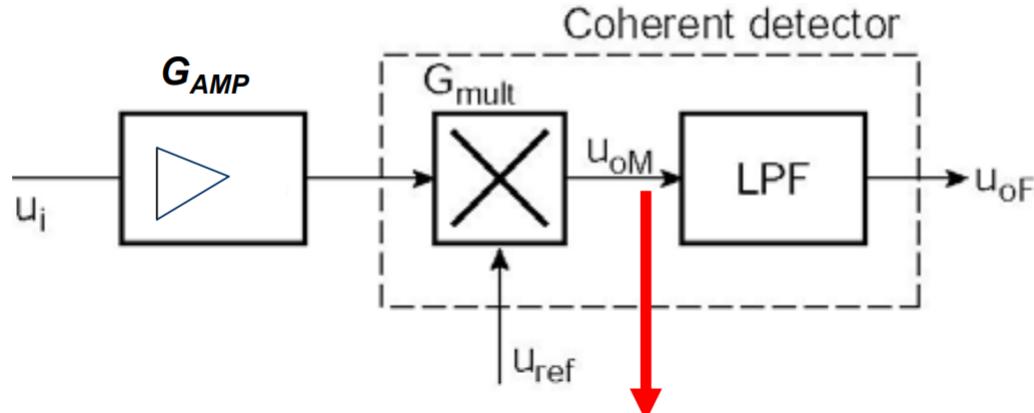A coherent detector behaves like a bandpass filter



$$u_{oM} = G_{Amp} G_{mult} [\hat{u}_i \sin(\omega_i t) \hat{u}_r \sin(\omega_r t)]$$


$$u_{oM} = G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos((\omega_r - \omega_i)t) - \cos((\omega_r + \omega_i)t)]$$

Now if: $\omega_r = \omega_i$ (Coherent signals !) then:

$$u_{oM} = G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [1 - \cos(2\omega_i t)]$$

DC

Amplitude detection

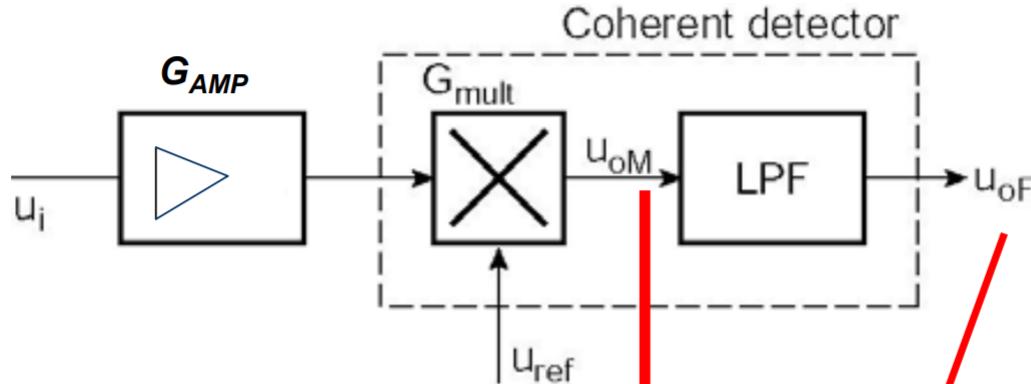

$$u_{oM} = G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [1 - \cos(2\omega_i t)]$$

$\omega_r = \omega_i$

The low-pass filter removes the second harmonic:

$$u_{oF} = G_{LPF} G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2}$$

This coherent detector detects the **amplitude** of the input signal.


Note that **in this case U_i and U_{ref}** are in-phase (Synchronous detection).

What if they are not in-phase ????

Phase detection

ET8.017
El. Instr.

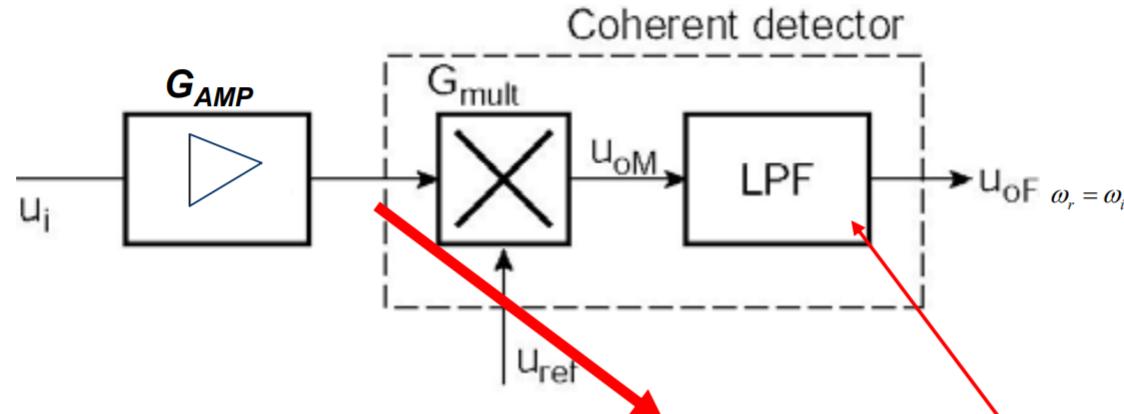Suppose U_i and U_{ref} have a phase difference:



$$u_{oM} = G_{Amp} G_{mult} [\hat{u}_i \sin(\omega_i t + \varphi) \hat{u}_r \sin(\omega_r t)]$$

$$u_{oM} = G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos((\omega_r - \omega_i)t + \varphi) - \cos((\omega_r + \omega_i)t + \varphi)]$$

$$u_{oF} = G_{LPF} G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos(\varphi)] = 0$$


This coherent detector is also **phase sensitive**.

Coherent detection in practice

ET8.017
El. Instr.


Linear operation of an analog multiplier circuit, working over a large range of input signals is difficult to realize in practice.

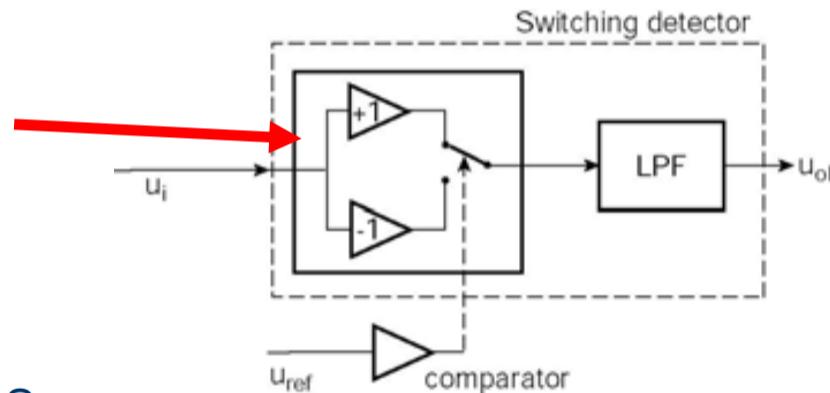A much simpler realization is a switching detector a.k.a. a **chopper**




Chopper realization in CMOS:

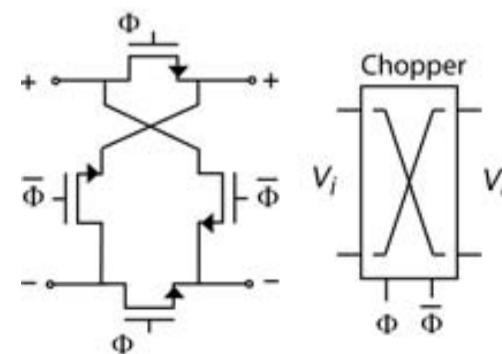Easy: just 4 transistors!
 Accurate: does not introduce offset
 But: switching spikes can cause problems (residual offset)




Summary

ET8.017
El. Instr.

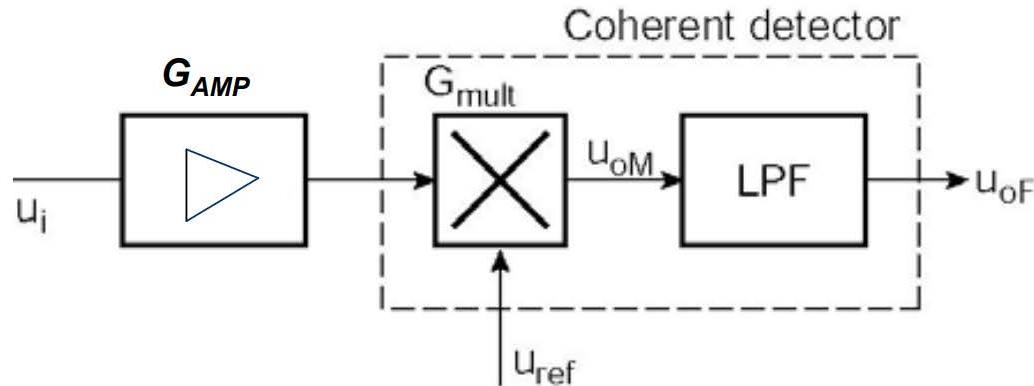

REMEMBER:

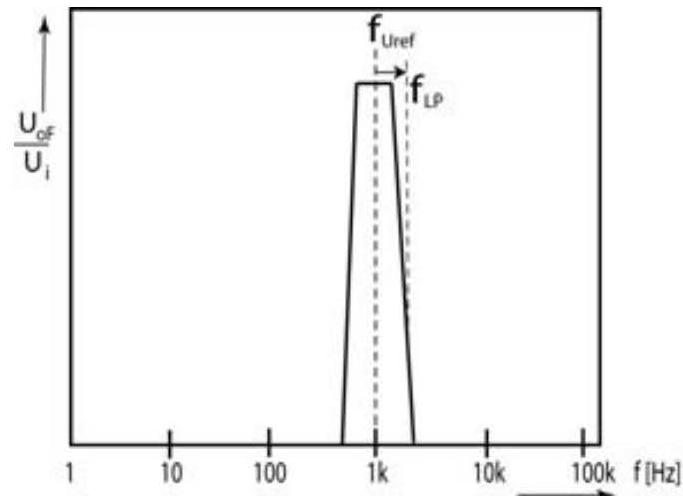
- An ideal coherent detector is only sensitive to frequency components in a narrow band around a reference signal U_{ref} .
- The low-pass filter determines the signal bandwidth



So what happens if U_{ref} is a square wave ??

DEMO: Coherent detection for the readout of strain-gauges

ET8.017
El. Instr.

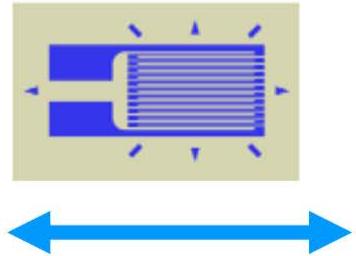

R is typically 100-2000 Ω


ΔR is typically 10^{-1} - 10^{-5} Ω

Very small changes in resistance
should be measured



Wheatstone ½ bridge

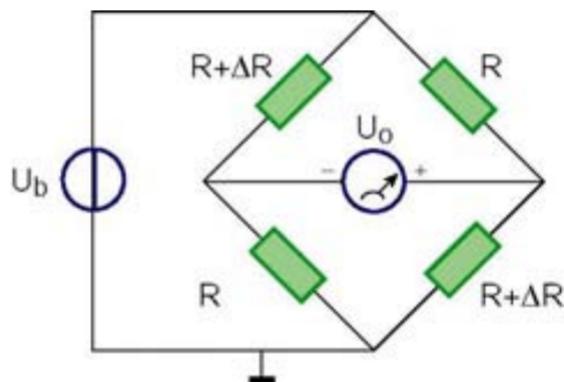Construction enables only stressed and non-stressed strain gauges



$$U_{o+} = \frac{R + \Delta R}{(R + \Delta R) + R} U_b = \frac{R + \Delta R}{2R + \Delta R} U_b$$

$$U_{o-} = \frac{R}{(R + \Delta R) + R} U_b = \frac{R}{2R + \Delta R} U_b$$

$$U_d = U_{o+} - U_{o-} = \frac{\Delta R}{2R + \Delta R} U_b$$

Non-linearity error is small if $\Delta R \ll 2R$

U_b can be an AC source of well-known frequency
 U_o is a very small AC signal (typically a few uV)

with a high noise level !


Some data:

Strain gauges : 120 ohm, length 6mm
Steel bar: area = 1cm²

1 kg gives: $\Delta l = 2,86 \text{ nm}$

Resistance change: $\Delta R = 120 \mu\Omega$

Relative change: $\Delta R/R = 10^{-6}$

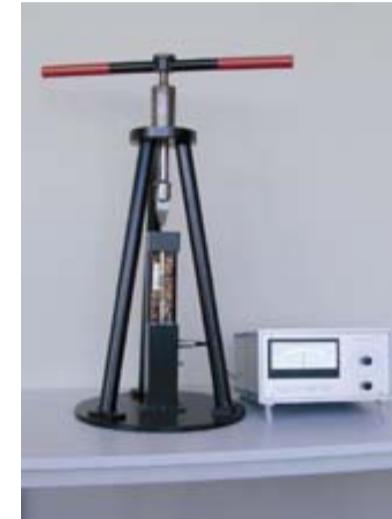


Noise level:

Force: 10N , or 1kg


Max force: 15 kN, or 1500 kg (Steel bar limit)

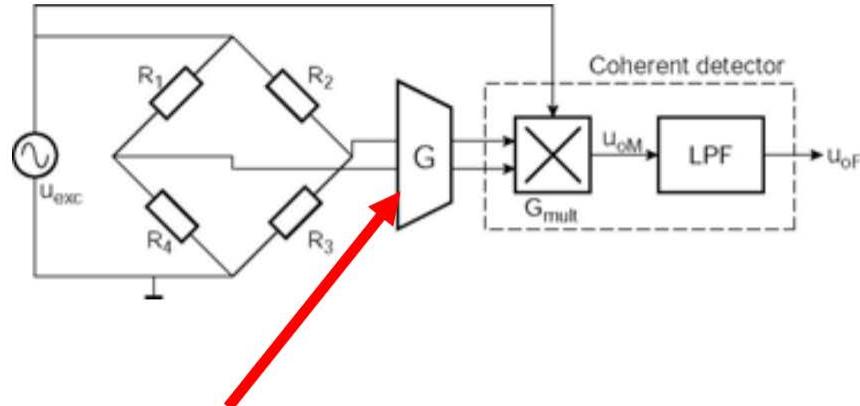Dynamic range: $1500/0.1 = 15*10^3 = 84 \text{ dB}$




Use an AC amplifier

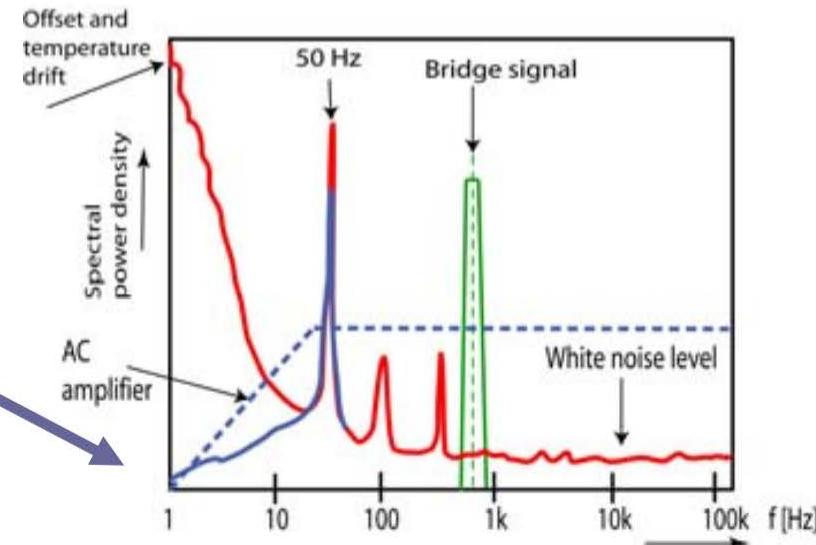Offset suppression
reduces overload on
multiplier



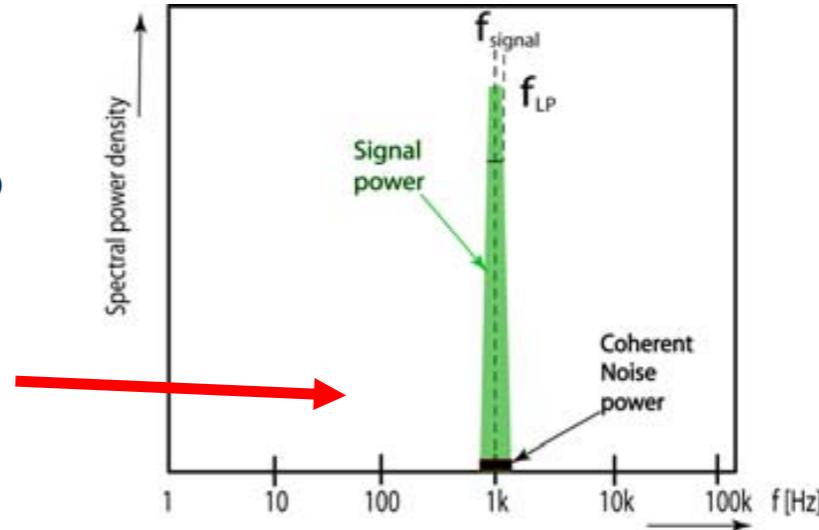Signal-Noise ratio
=
Green area
Black area




Other detection limits are due to:

- o Offsets in both input- and output channel
- o Non-linearities in the reference channel
- o Non-linearities in the input channel
- o Non-linearities at the output of the multiplier

Lock-in amplifier

ET8.017
EI. Instr.

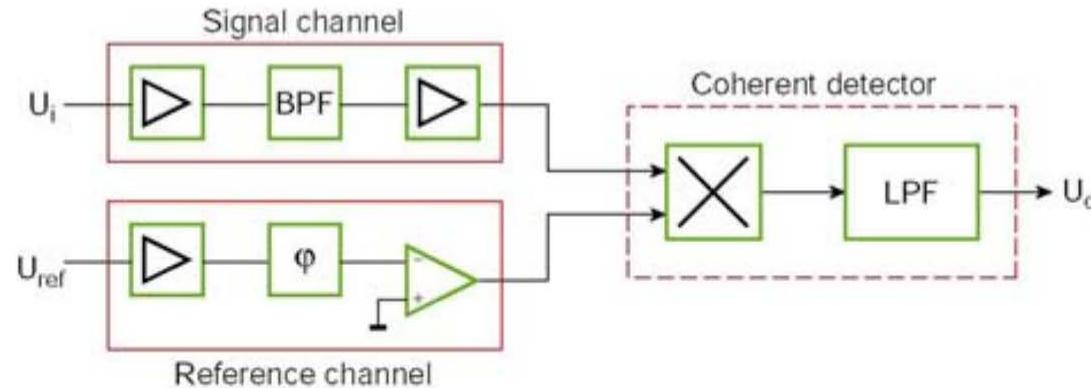A lock-in amplifier is a coherent detector with all the extra features required of a general-purpose laboratory instrument.



Source: LED modulated with a sine wave

Detector: Photodiode

Instrument: Analog lock-in amplifier (PAR 186)


Interference:

Ambient light, DC (offset), 50 Hz mains (lamp)

PLL for recovery of excitation voltage

ET8.017
El. Instr.

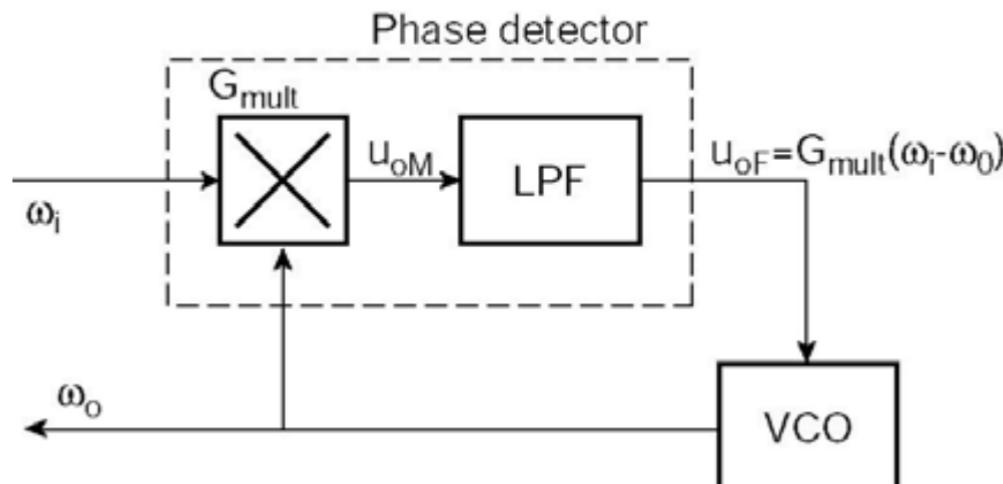The excitation frequency of remote sensors is not always directly available, but can be retrieved from the sensor's output signal by a phase-locked loop (PLL).




The loop drives the VCO so as to minimize the error signal U_{oM}
As a result, $\omega_i \sim \omega_o$ with a small loop-gain-dependent phase error

Digital lock-in amplifier

ET8.017
El. Instr.

Analog functionality is replaced by digital signal processing (DSP)

⇒ Cost, Flexibility, User friendliness

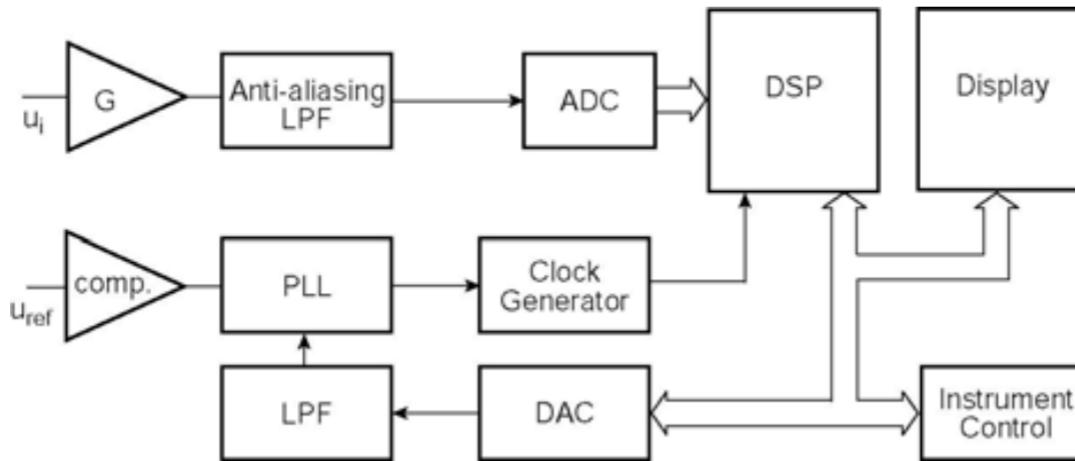

ADC and DSP are critical (frequency limiting) components

Digital lock-in amplifiers are becoming more and more economical and common in test-setups in the lab and in industry

Summary

ET8.017
EI. Instr.

Coherent detection is a powerful technique to accurately measure low-level periodic signals in the presence of high levels of noise and interference.

Both amplitude and phase can be measured

The signal frequency should be known (reference channel) or it should be possible to regenerate it with a PLL.

The operating frequency should be in a frequency band where disturbing signals and noise are low.

Distortion in the input- or reference channel can lead to harmonic sensitivity

Modern (digital) lock-in amplifiers can also measure the amplitude and phase of harmonic signals ($2f$, $3f$, $4f$ etc.) e.g. for the measurement of signal distortion.